

عنوان المحاضرة: Zener Diode



جامعة ساوة

كلية التقنية الهندسية

القسم الاجهزة الطبية

المرحلة الثانية

رقم المحاضرة السادسة

اسم المحاضر م.م احمد عذافه كريم

Zener Diode

The Zener diode acts just like a normal diode when forward biased, but when a reverse voltage is applied, the voltage across it remains constant, where that happens when the applied reverse voltage is higher than the Zener voltage V_z .


Reverse voltage can be increased even after the breakdown voltage is reached. **At this point, maximum current will flow through the Zener diode. This breakdown point is referred to as “Zener voltage”.**

From the I-V Characteristics, we see that the Zener diode has a region in its reverse bias half (left half) in which there is a constant negative voltage even with large changes in current.

This is true as long as the Zener diode current remains between the minimum breakdown current $I_{Z(\min)}$ and the maximum current $I_{Z(\max)}$.

This ability can be used to regulate a voltage source against supply voltage changes.

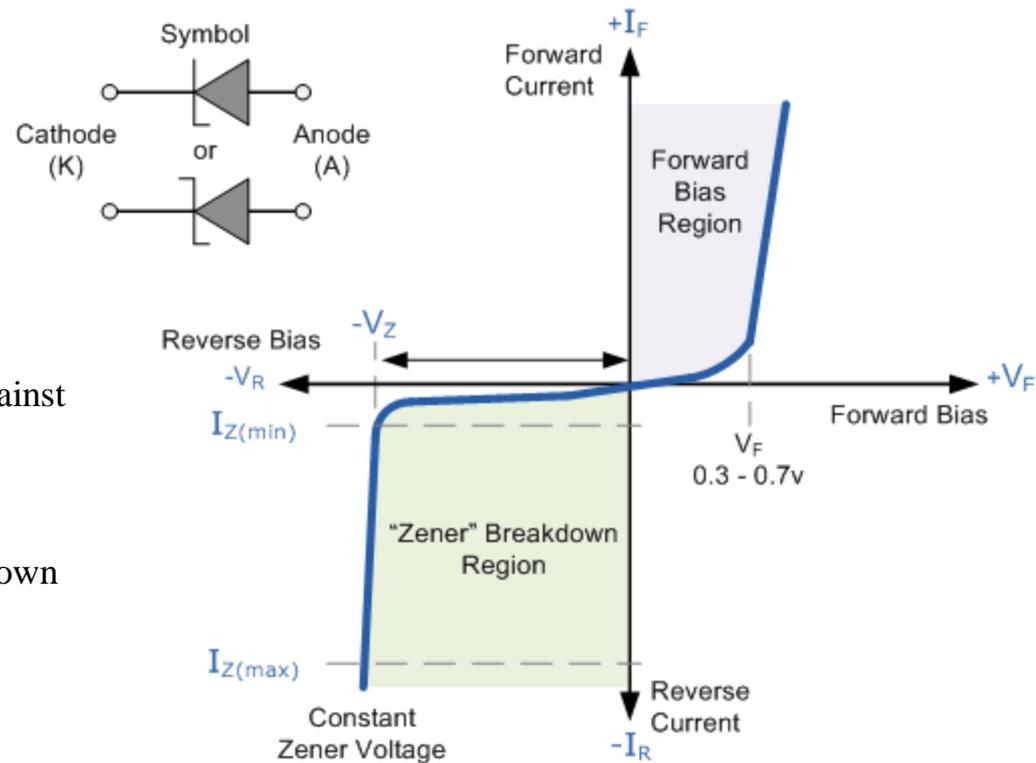The fact that the voltage across the diode in the breakdown region is almost constant is an important application of the Zener diode as a (voltage regulator).




The Zener Diode Regulator circuit

For the circuit, the resistor R_S is connected in series with the Zener diode to limit the current flow. The stabilized output voltage V_{out} is taken from across the Zener diode. The Zener diode is connected such that its - terminal is connected to the positive terminal of the DC supply, so it is reverse biased.

The load is connected in parallel with the Zener diode, so the voltage across R_L is always the same as the Zener voltage, ($V_R = V_Z$). **There is a minimum Zener current for which the regulation of the voltage is active, where the Zener current must stay above this value. The supply voltage V_S must be greater than V_Z .**

A Zener diode is always operated in its reverse biased mode. **A voltage regulator circuit can be designed using a Zener diode, and it is used to maintain a constant DC output voltage across the load, which is done in spite of changes in the input voltage, or changes in the load current.** The Zener voltage regulator consists of a current limiting resistor R_S connected in series with the input voltage source V_S , and the Zener diode is connected in parallel with the load R_L in this reverse biased condition. **The stabilized output voltage is always the same as the breakdown voltage V_Z of the diode.**

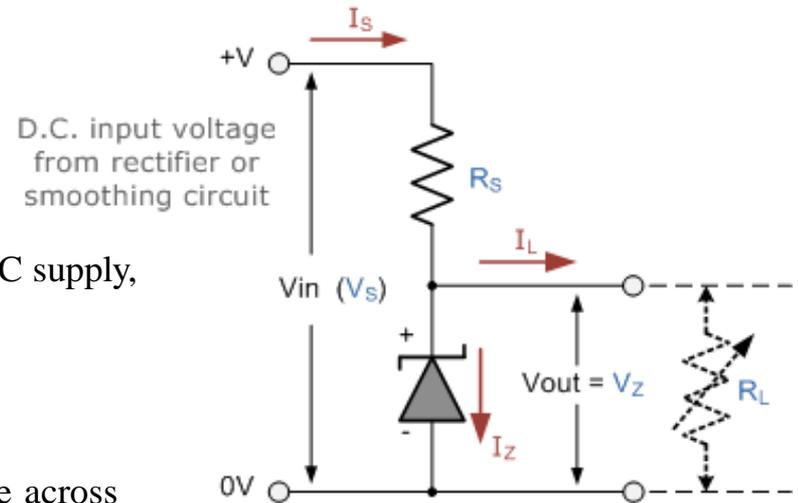

Example on The Zener Diode Regulator

A voltage source of about 5 V is required to be produced from a 12 V DC voltage source. The maximum power rating P_Z of the Zener diode is 2 W. Using the Zener regulator circuit shown previously, calculate:

a). The maximum current flowing through the Zener diode:


$$\text{Maximum Current} = \frac{\text{Watts}}{\text{Voltage}} = \frac{2\text{w}}{5\text{v}} = 400\text{mA}$$

b). The minimum value of the series resistor, R_S

$$R_S = \frac{V_S - V_Z}{I_Z} = \frac{12 - 5}{400\text{mA}} = 17.5\Omega$$

c). The load current I_L if a load resistor of $1\text{k}\Omega$ is connected across the Zener diode.
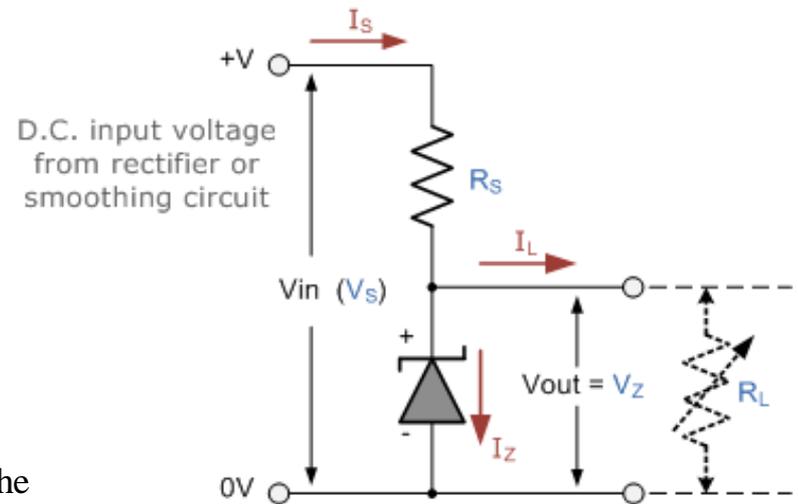
$$I_L = \frac{V_Z}{R_L} = \frac{5\text{v}}{1000\Omega} = 5\text{mA}$$



Notes:

- 1- The max. current passing through the Zener ($I_{Z_{max}}$) occur when the load current is zero.
- 2- The min. value for the series resistance can be calculated when the max. current pass through the Zener.