



جامعة ساوة الاهلية

كلية التقنيات الهندسية

القسم: الفيزياء الطبية والعلاج الاشعاعي

المرحلة الثانية / الفصل الثاني

عنوان المحاضرة:

Bipolar Junction transistor (BJT)

رقم المحاضرة (7)

اسم المحاضر: عطالله باني حمود

The Seventh lecture/ twelveth week

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ
IN THE NAME OF GOD, THE MOST
GRACIOUS, THE MOST MERCIFUL

**Department of Physics
and Radiotherapy**


Bipolar Junction transistor (BJT)

Transistor Definition

A transistor is a semiconductor device used to amplify or switch electrical signals and power. It is one of the basic building blocks of modern electronics.[1] It is composed of semiconductor material, usually with at least three terminals for connection to an electronic circuit.


- (a) collector : It is the largest part and dissipates heat.
- (b) emitter : It is emitting electrons through the base to the collector.
- (c) base : It is thinner and smaller in size and located between the collector and emitter

UNBIASED TRANSISTOR

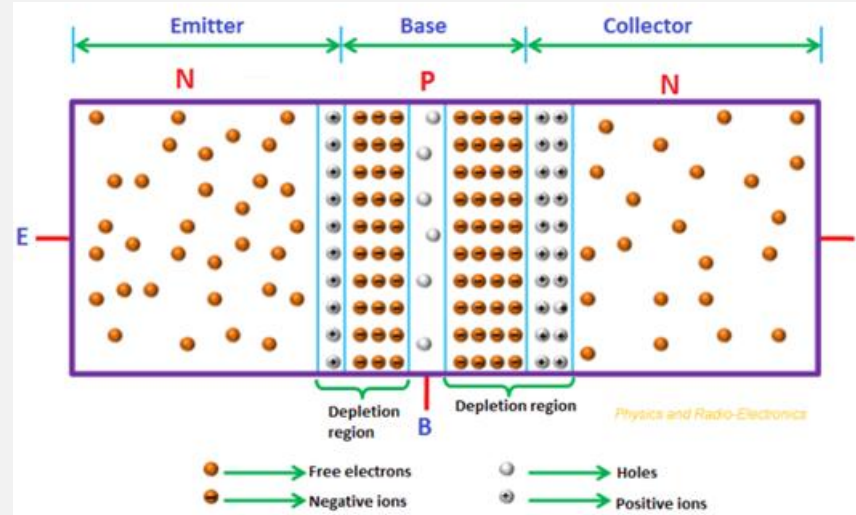

Transistor symbol:

Fig. (30)Tansistor Types

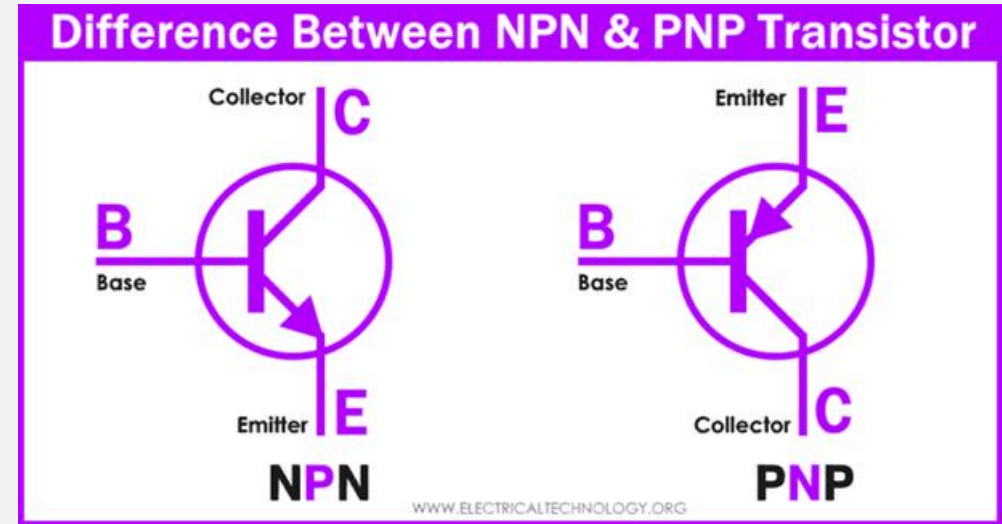

Configuration of Transistor

The three types of configurations are

- (a) **Common Base configuration**
- (b) **Common Collector configuration**
- (c) **Common Emitter configuration**

In every configuration, the emitter junction is forward biased and the collector junction is reverse biased.

(a) Common Base CB Configuration

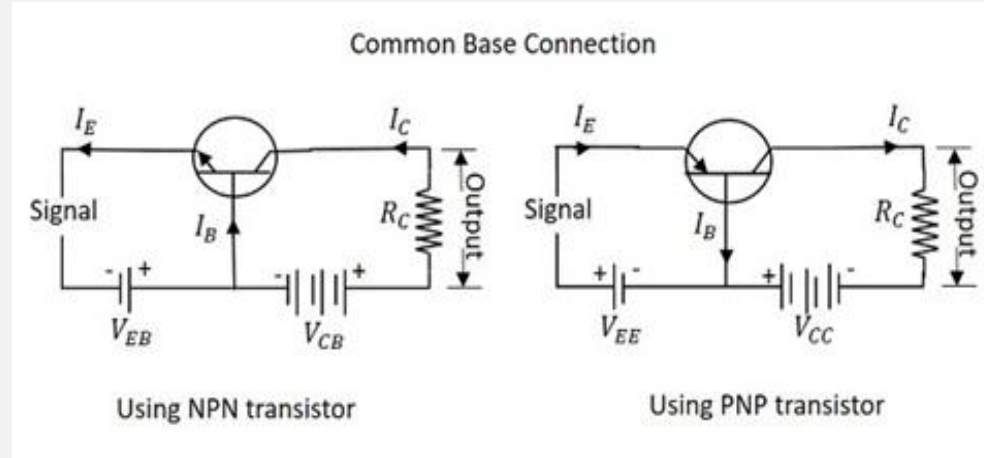


Fig. (32) Common Base con.

(b) Common Collector CC Configuration

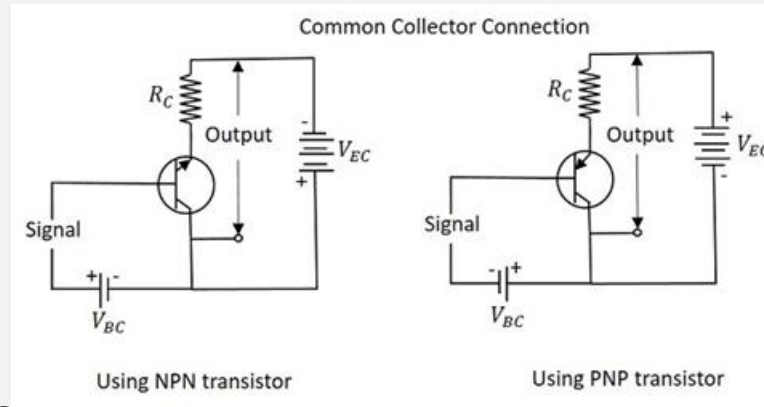


Fig. (33) Common collector con.

(c) Common Emitter configuration

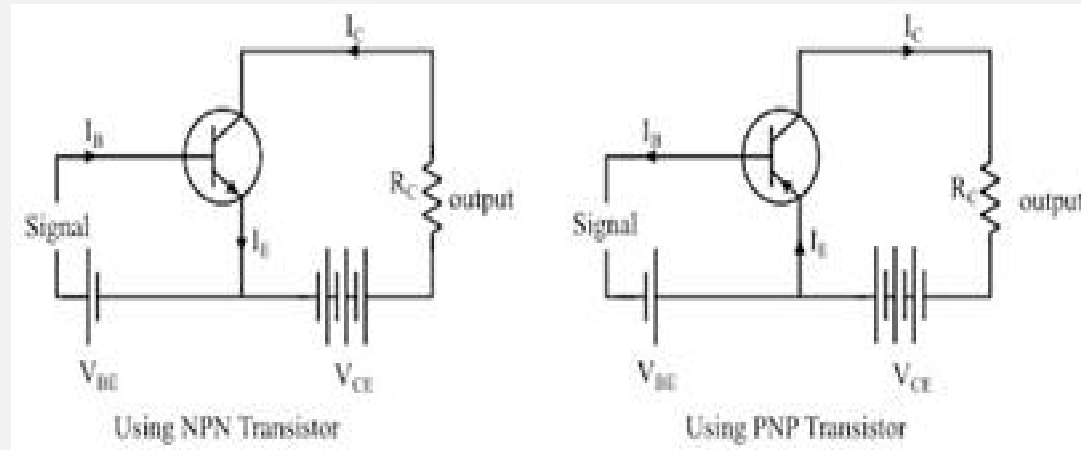


Fig. (34) Common Emitter

Type equation here. **Base Current Amplification factor** β

$$\beta = \frac{\Delta I_c}{\Delta I_B} \text{ or } \beta = \frac{I_c}{I_B} \text{ -----(38)}$$

Type equation here. **Emitter Current Amplification factor** α

$$\alpha = \frac{\Delta I_c}{\Delta I_E} \text{ -----(39)}$$

$$I_E = I_c + I_B \text{ -----(40)}$$

$$\Delta I_E = \Delta I_c + \Delta I_B \text{ -----(41)}$$

Relation between β and α

When we divide equation (41) by (ΔI_c) we obtain :

$$\Delta I_E = \Delta I_c + \Delta I_B \quad \text{-----(41)}$$
$$\frac{\Delta I_E}{\Delta I_c} = \frac{\Delta I_c}{\Delta I_c} + \frac{\Delta I_B}{\Delta I_c} \quad \text{from equation (39) and (38) we obtain :}$$

$$\begin{aligned} \frac{1}{\alpha} &= 1 + \frac{1}{\beta} \\ \frac{1}{\alpha} - 1 &= \frac{1}{\beta} \\ \frac{1-\alpha}{\alpha} &= \frac{1}{\beta} \quad \text{-----(42)} \end{aligned}$$

When we reverse the equation (42) :

$$\beta = \frac{\alpha}{1-\alpha} \quad \text{-----(43)}$$

$$\alpha = \frac{\beta}{1+\beta} \quad (\text{Home Work})$$

Different Regions of BJT Operation

Fig.(35) (CE-Configuration of BJT)

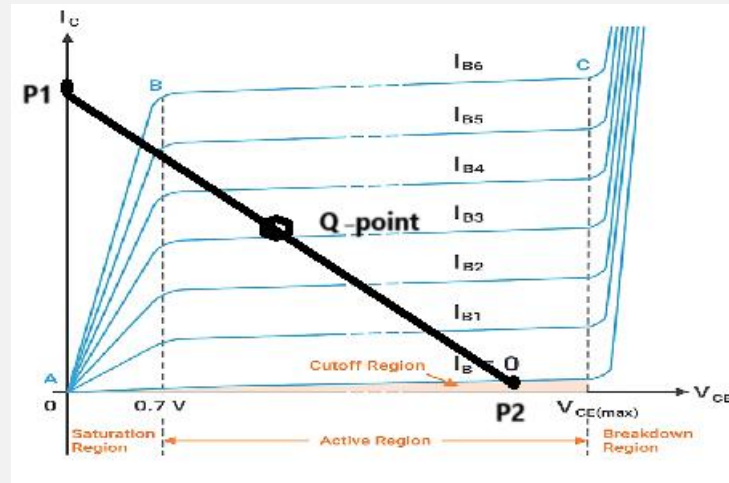
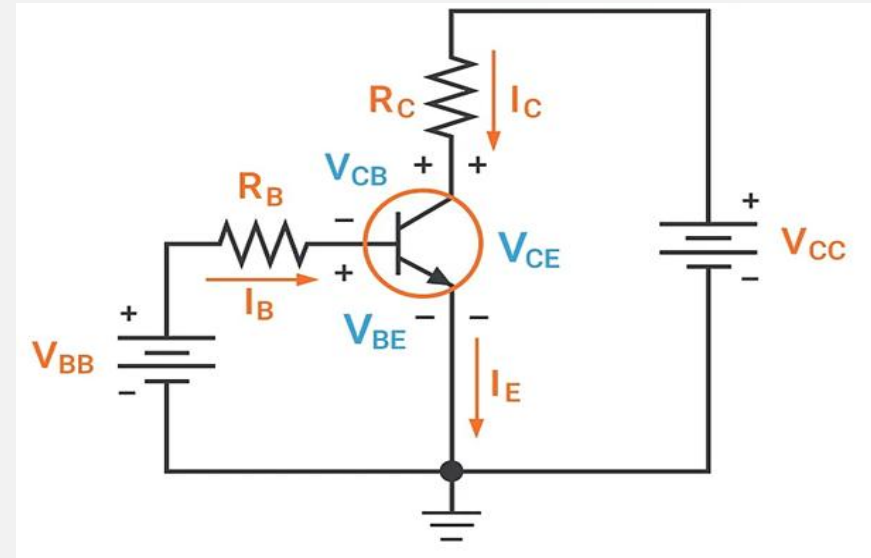


Fig.(36) BJT Operation region

(a) Cut- off region:

In this region

1- ($I_B = 0\text{ A}$) see equation (38) ,Hence

2- ($I_C = 0\text{ A}$)

3- $V_{CE} = V_{CC}$

(b) Saturatiion region:

In this region

1- ($I_B = \text{Maximum Value}$) see equation (38) ,Hence

2- ($I_C = I_{\text{saturation current A}}$)

3- $V_{CE} = 0\text{ v}$

(c) Operation Region:

In this region, The emitter diode is forward

Baised, while the collector diode is reverse baised

Here, all variables (I_B , I_C , V_{CE}) have specific values

انتہی شکرا لاستماعکم